

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
FOURTH SEMESTER B.TECH DEGREE EXAMINATION(R&S), MAY 2019

Course Code: EC204

Course Name: ANALOG INTEGRATED CIRCUITS (AE, EC)

Max. Marks: 100

Duration: 3 Hours

PART A

Answer any two full questions, each carries 15 marks.

- | | | Marks |
|---|--|-------|
| 1 | a) Derive the equation for closed loop voltage gain, input resistance with feedback, output resistance with feedback and total output offset voltage with feedback of a voltage series feedback amplifier. | (10) |
| | b) Define slew rate. What are its causes? Derive the equation for maximum input frequency at which an undistorted signal is obtained in terms of slew rate? | (5) |
| 2 | a) Design an inverting adder circuit using opamp to get the output expression as $V_0 = -(0.2V_1 + 2V_2 + 20V_3)$, where V_1 , V_2 and V_3 are the inputs. | (7) |
| | b) Derive the equation for the output voltage for an averaging circuit using opamp. | (8) |
| 3 | a) Draw the equivalent circuit of an operational amplifier. Explain voltage transfer characteristics of an operational amplifier. | (8) |
| | b) Define a) Power Supply Rejection Ratio b) Input Offset Current | (7) |

PART B

Answer any two full questions, each carries 15 marks.

- | | | |
|---|--|------|
| 4 | a) Explain the working of full wave precision rectifier. | (9) |
| | b) Derive the equation for output voltage of an integrator. Why is it called a lossy integrator? | (6) |
| 5 | a) Explain how switching takes place at UTP and LTP in a Schmitt trigger. Plot the hysteresis curve. | (10) |
| | b) What is a zero crossing detector? | (5) |
| 6 | a) Design a first order low pass filter at a cut-off frequency of 2kHz with a pass band gain of 3 | (8) |
| | b) Prove that the input voltage is converted into corresponding output current in a voltage to current converter with floating load. | (7) |

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) Explain the operation of Phase Locked Loop. What is lock range and capture range? (10)
- b) With the help of internal diagram explain the monostable operation of timer IC 555. Draw the input and different output waveforms. Derive the equation for pulse width. (10)
- 8 a) Explain the working of successive approximation ADC (10)
- b) Discuss the operation of dual slope ADC (10)
- 9 a) What is a sample and hold circuit (5)
- b) Discuss how digital signal is converted into analog signal in a weighted resistor DAC. (6)
- c) Explain the internal diagram of I.C. 723 (6)
- d) Explain how current boosting is achieved using I.C 723 (3)

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
FOURTH SEMESTER B.TECH DEGREE EXAMINATION, APRIL 2018

Course Code: EC204

Course Name: ANALOG INTEGRATED CIRCUITS (AE, EC)

Max. Marks: 100

Duration: 3 Hours

PART A

Answer any two full questions, each carries 15 marks.

Marks

- | | | |
|---|---|-----|
| 1 | a) Derive CMRR, input resistance and output resistance of a dual input balanced output differential amplifier configuration. | (8) |
| | b) Define the following: | (3) |
| | i) Input bias current ii) Input offset current iii) Input offset voltage | |
| | c) Implement the equation using two op-amps
$V_0 = -5V_1 + 2V_2 - 10V_3$ | (4) |
| 2 | a) Derive the following characteristics of voltage shunt amplifier: | (8) |
| | i) Closed loop voltage gain ii) Input resistance | |
| | iii) Output resistance iv) Bandwidth | |
| | b) What is slew rate? Derive an equation for it. | (4) |
| | c) A differential amplifier has a common mode gain of 0.05 and difference mode gain of 1000. Calculate the output voltage for two signals $V_1 = 1\text{mV}$ and $V_2 = 0.9\text{mV}$ | (3) |
| 3 | a) Explain the variation of differential gain of a differential amplifier with frequency of operation with relevant expressions. | (5) |
| | b) Draw the circuit diagram of a differential instrumentation amplifier with a transducer bridge and show that the output voltage is proportional to the change in resistance. | (7) |
| | c) How a constant current bias circuit can be used to improve the CMRR of a differential amplifier? | (3) |

PART B

Answer any two full questions, each carries 15 marks.

- | | | |
|---|--|-----|
| 4 | a) Draw the circuit of a temperature compensated logarithmic amplifier and show that it provides temperature independent logarithmic output. | (8) |
| | b) Explain the working of a triangular waveform generator with a neat circuit diagram. Also derive an expression for frequency of oscillation. | (7) |
| 5 | a) Draw the circuit of a Wien Bridge oscillator using op-amp and derive an equation for frequency of oscillation. | (7) |
| | b) With a neat circuit diagram explain the working of astable multivibrator using op-amp. Also derive an expression for time period. | (8) |
| 6 | a) Draw the circuit of second order low pass filter and derive its transfer function. | (8) |
| | b) Draw the circuit of a precision full-wave rectifier and explain its working. | (7) |

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) Explain how a monostable multivibrator can be implemented with 555 IC with relevant waveforms and functional diagram. Derive an expression for pulse width. (10)
b) With a neat circuit diagram, explain the operation of a 3-bit flash converter. (10)
- 8 a) With a neat block diagram explain the working of PLL. Explain any two applications of PLL. (10)
b) Explain the working of dual-slope ADC with a neat circuit diagram. (10)
- 9 a) Explain how short circuit, fold back protection and current boosting are done using IC723 voltage regulator. (10)
b) With a neat circuit diagram explain the working of a weighted resistor D/A converter (10)



Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
FOURTH SEMESTER B.TECH DEGREE EXAMINATION, JULY 2017

Course Code: EC204

Course Name: ANALOG INTEGRATED CIRCUITS (AE, EC)

Max. Marks: 100

Duration: 3 Hours

PART A

Question No.1 is compulsory. Answer question 2 or 3

- 1 a) Draw the block diagram of an op-amp and explain the necessity and implementation of each block. (10)
 - b) Design an op-amp based circuit to implement the function, $V_o = 2V_a + 3V_b$. (5)
 - 2 a) With suitable diagram explain how the voltage series feedback is implemented in op-amp based circuits. (5)
 - b) Derive the expressions for gain, input impedance, output impedance and frequency response of the above configuration. (10)
- OR**
- 3 a) Draw and explain the circuit diagram of an instrumentation amplifier and derive the output equation. (10)
 - b) With suitable diagram and equation, explain how the average of signals can be achieved by using an op-amp circuit. (5)

PART B

Question No.4 is compulsory. Answer question 5 or 6

- 4 a) Design an op-amp based astable multi-vibrator for a duty cycle of 75% and draw the waveforms at different points. (8)
 - b) Draw and explain the circuit diagram of a log amplifier and derive the output equation. (7)
 - 5 a) Draw and explain the working of a practical differentiator circuit including frequency response analysis. (15)
- OR**
- 6 a) Design a Schmitt trigger circuit for different UTP and LTP magnitudes. (7)
 - b) Draw and explain the circuit of a square/saw tooth wave generator using op-amps. (8)

PART C

Question No.7 is compulsory. Answer question 8 or 9

- 7 a) List the features of IC555 and design a monostable multi-vibrator for a pulse duration of 1ms using IC555. (10)
 - b) With suitable diagram explain the working of a flash convertor. (10)
 - 8 a) Draw and explain the working of a PLL and describe the importance of lock range and capture range. (10)
 - b) Explain the method of current boosting in voltage regulator IC's. (10)
- OR**
- 9 a) Draw and explain the working of a binary ladder type D/A convertor. (10)
 - b) List and explain at least five important specifications of D/A and A/D convertors. (10)

Reg. No. _____ Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
FOURTH SEMESTER B.TECH DEGREE EXAMINATION, JUNE 2017

Course Code: **EC204**Course Name: **ANALOG INTEGRATED CIRCUITS (AE, EC)**

Max. Marks: 100

Duration: 3 Hours

PART A*Question No.1 is compulsory. Answer question 2 or 3*

1. a. Define the following terms (6)
 - i) CMRR
 - ii) Slew rate
 - iii) PSRR
- b. Design a circuit to obtain an output voltage of $-(V_1 + 2V_2 + 5V_3)$ (5)
- c. Derive the following characteristics of voltage series feedback amplifier. (4)
 - i) Closed loop gain
 - ii) Input impedance
 - iii) Output impedance
 - iv) Bandwidth
2. a. Explain in detail a method of improving CMRR of differential amplifier. (10)
- b. Explain the various stages of op-amp. (5)

OR

3. Draw an instrumentation amplifier using four op-amps and explain the need for each op-amp. Derive the expression for its output voltage. (15)

PART B*Question No.4 is compulsory. Answer question 5 or 6.*

4. a. Explain the working of precision full wave rectifier with a neat diagram. (7)
- b. Draw a second order active high pass filter and derive the expression for its cut off frequency. (8)
5. a. With the help of a neat diagram, derive the frequency of oscillation for RC phase shift oscillator. (10)
- b. Draw the circuit of antilog amplifier and derive the output voltage. (5)

OR

6. a. Explain in detail the working of Schmitt trigger and explain the transfer characteristics. (8)
- b. Design a first order low pass filter with a cut off frequency of 2kHz. (7)

PART C

Question No.7 is compulsory. Answer question 8 or 9.

7. a. Discuss in detail any two applications of PLL. (5)
- b. Write a short note on IC723 based voltage regulators (5)
- c. Explain the working of dual slope A/D converters. (10)
8. a. Explain in detail the working of monostable and astable multivibrator using 555. (10)
- b. Discuss different methods for implementing analog multipliers. (5)
- c. Explain the working of high speed sample and hold switch. (5)

OR

9. a. Derive the output voltage for a 4 bit R-2R ladder D/A converters (10)
- b. Explain the working of successive approximation type A/D converters. (7)
